



## Lab Experiment #4:

# Wheatstone Bridge

David McNeary

Partner: Glendy Lara

PHYS 200BL

10/4/2021

## Data

### Measurement of $R_1$

	Iteration 1	Iteration 2	Iteration 3	Iteration 4	Iteration 5
$R_s$	$15\Omega$	$50\Omega$	$70\Omega$	$85\Omega$	$30\Omega$
$x$ (cm)	68.1 cm	41.6 cm	29.7 cm	35.8 cm	50.1 cm
$R_1$	$32\Omega$	$36\Omega$	$30\Omega$	$47\Omega$	$30\Omega$

Direct multimeter measurement:  $59.8\Omega$

### Measurement of $R_2$

	Iteration 1	Iteration 2	Iteration 3	Iteration 4	Iteration 5
$R_s$	$15\Omega$	$30\Omega$	$50\Omega$	$70\Omega$	$23\Omega$
$x$ (cm)	63.9 cm	45.6 cm	33.5 cm	26.6 cm	52.2 cm
$R_2$	$27\Omega$	$25\Omega$	$25\Omega$	$25\Omega$	$25\Omega$

Direct multimeter measurement:  $28.4\Omega$

# Data Reduction

	$x$	$R$	$\Delta x$	$\Delta R$
$R_1$	50.1 cm	$30\Omega$	0.1 cm	$0.1\Omega$
$R_2$	52.2 cm	$25\Omega$	2.2 cm	$2.3\Omega$

## Lab Questions

- Using formula 4.5 and "percent difference" formula to calculate percent uncertainty:

a.  $x = 10 \pm 0.1$  cm:

$$100 \left[ \frac{\left| 40.1 \frac{100}{(100-9.9)^2} - 39.9 \frac{100}{(100-10.1)^2} \right|}{\frac{40.1 \frac{100}{(100-9.9)^2} + 39.9 \frac{100}{(100-10.1)^2}}{2}} \right] = 0.56\%$$

b.  $x = 50 \pm 0.1$  cm

$$100 \left[ \frac{\left| 0.1 \frac{100}{(100-49.9)^2} - 0.1 \frac{100}{(100-50.1)^2} \right|}{\frac{0.1 \frac{100}{(100-49.9)^2} + 0.1 \frac{100}{(100-50.1)^2}}{2}} \right] = 0.80\%$$

c.  $x = 95 \pm 0.1$  cm

$$100 \left[ \frac{\left| 45.1 \frac{100}{(100-94.9)^2} - 44.9 \frac{100}{(100-95.1)^2} \right|}{\frac{45.1 \frac{100}{(100-94.9)^2} + 44.9 \frac{100}{(100-95.1)^2}}{2}} \right] = 7.55\%$$

- If the 2 volts from the power supply were to be increased to 6 volts, I would expect the galvanometer to be much more sensitive to minute movements in the position of the "split" of the wire of the potentiometer ( $x$  vs  $100 - x$ ), since given the same amount of resistance from the components of the circuit, there would be more current flowing (following from Ohm's Law). Since the galvanometer reads in  $\mu\text{A}$ ,

we would need to be careful in using the "K-key" to increase the accuracy of the reading. to avoid overloading the galvanometer. I might also expect the wire of the potentiometer to get quite hot.

3. Depressing the K-key of the galvanometer greatly increased the precision of the reading once we were in the "ballpark" of a good  $x$ —value for an accurate reading. However, this increased sensitivity provided some concern when the distance to a proper  $x$  was increased, as the instrument is apparently quite vulnerable to current in an "unbalanced" circuit.
4. Fluctuations in the voltage provided by the power supply will result in a fluctuating current reading from the galvanometer, and will make it harder to pinpoint a "balance" point for the  $x$ —position of the right and left sides of the split potentiometer resistance.
5. The contact point should be moved towards the right, decreasing the  $x$  distance.
6. The measured and observed values for  $R_2$  are quite close, and the percent difference is quite small:


$$100 \left[ \frac{|25\Omega - 28.4\Omega|}{\frac{25\Omega + 28.4\Omega}{2}} \right] = 8.7\%$$

However, the results from observed vs. direct measurements of  $R_1$  are inconclusive, given the large percent of error:

$$100 \left[ \frac{|30\Omega - 59.8\Omega|}{\frac{30\Omega + 59.8\Omega}{2}} \right] = 66\%$$

---

## Data sheet + Quiz

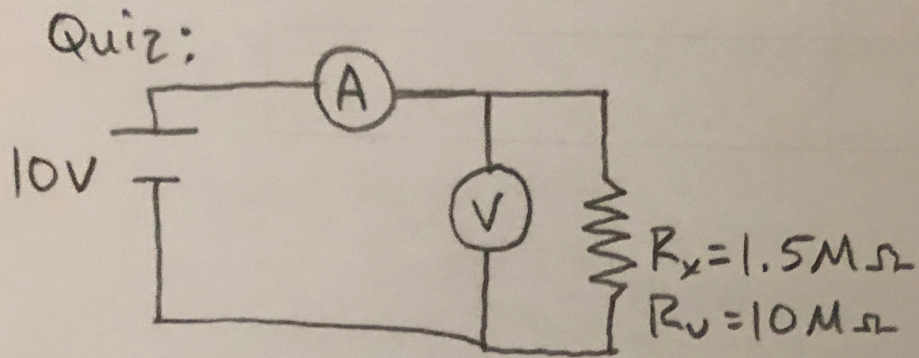

$$V = IR$$

$$\frac{V}{R} = I \rightarrow R = \frac{R_x R_v}{R_x + R_v} \rightarrow \frac{V(R_x + R_v)}{R_x R_v} = I$$

$$I = \frac{10\text{V}(11.5 \text{ M}\Omega)}{15 \text{ M}\Omega}$$

$$I = 7.7 \text{ A}$$



## 4.7 Data sheet

Name: <i>David McNeary</i>	Date: <i>10/4/21</i>	Instructor's initials:
Partner: <i>Glendy Lara</i>	Group No:	

## Data

Measurement of the resistance  $R_1$ .

Iterate as described in section 4.5

	1	2	3	4	5
$R_s$	<i>15 <math>\Omega</math></i>	<i>50 <math>\Omega</math></i>	<i>70 <math>\Omega</math></i>	<i>85 <math>\Omega</math></i>	<i>30 <math>\Omega</math></i>
x (cm)	<i>68.1 cm</i>	<i>41.6 cm</i>	<i>29.7 cm</i>	<i>35.8 cm</i>	<i>50.1 cm</i>
$R_1$ (eq 4.4)	<i>32 <math>\Omega</math></i>	<i>30.8 <math>\Omega</math></i>	<i>30 <math>\Omega</math></i>	<i>47 <math>\Omega</math></i>	<i>30 <math>\Omega</math></i>

Direct measurement of the resistance with the multi-meter:

$R_1$	<i>59.8 <math>\Omega</math></i>	$\pm$	
-------	---------------------------------	-------	--

Measurement of the resistance  $R_2$ 

Iterate as described in section 4.5

	1	2	3	4	5
$R_s$	<i>15 <math>\Omega</math></i>	<i>30 <math>\Omega</math></i>	<i>50 <math>\Omega</math></i>	<i>70 <math>\Omega</math></i>	<i>23 <math>\Omega</math></i>
x (cm)	<i>63.9 cm</i>	<i>45.6 cm</i>	<i>33.5 cm</i>	<i>26.6 cm</i>	<i>52.2 cm</i>
$R_2$	<i>27 <math>\Omega</math></i>	<i>25 <math>\Omega</math></i>	<i>25 <math>\Omega</math></i>	<i>25 <math>\Omega</math></i>	<i>25 <math>\Omega</math></i>

Direct measurement of the resistance with the multi-meter:

$R_2$	<i>28.4</i>	$\pm$	
-------	-------------	-------	--

## Data Reduction

Use the resistance values that you found closest to the center of the slide wire, i.e. closest to  $x = 50$  cm, record these below, and calculate the uncertainty in  $R$ ,  $\Delta R$ , using equation 4.5

	x	R	$\Delta x$	$\Delta R$
$R_1$	<i>50.1 cm</i>	<i>30 <math>\Omega</math></i>	<i>0.1 cm</i>	<i>0.1 <math>\Omega</math></i>
$R_2$	<i>52.2 cm</i>	<i>25 <math>\Omega</math></i>	<i>2.2 cm</i>	<i>2.3 <math>\Omega</math></i>